

# ELP201 Report

Uddhav Goel, 2019EE10540

May 2021

## 1 Synchronous 4-bit Gray-Code Counter

First, we start off by making the state transition table for our 4-bit gray-code counter, that covers all 16 states cyclically.

### 1.1 State Transition Table

$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3^N$	$Q_2^N$	$Q_1^N$	$Q_0^N$
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	1	0	0	1	0
0	0	1	0	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	0	1	0	1
0	1	0	1	0	1	0	0
0	1	0	0	1	1	0	0
1	1	0	0	1	1	0	1
1	1	0	1	1	1	1	1
1	1	1	1	1	1	1	0
1	1	1	0	1	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	1	0	0	1
1	0	0	1	1	0	0	0
1	0	0	0	0	0	0	0

Table 1: State transition table

## 1.2 Required Flip-Flops

Since we are building a 4-bit gray counter which has a total of 16 states

$\Rightarrow$  Minimum number of Flip-Flops required =  $\lceil \log_2 16 \rceil = 4$

Since we need an SR-flip flop to represent each bit and its transitions, we need **4 SR- Flip flops** for our 4-bit gray code counter.

## 1.3 Values of SR Flip-Flops

According to the state transition table shown in section 1.1, we get the following values that need to be assigned to the 4 SR-FFs, in order to implement the gray code counter.


$S_3$	$R_3$	$S_2$	$R_2$	$S_1$	$R_1$	$S_0$	$R_0$
0	x	0	x	0	x	1	0
0	x	0	x	1	0	x	0
0	x	0	x	x	0	0	1
0	x	1	0	x	0	0	x
0	x	x	0	x	0	1	0
0	x	x	0	0	1	x	0
0	x	x	0	0	x	0	1
1	0	x	0	0	x	0	x
x	0	x	0	0	x	1	0
x	0	x	0	1	0	x	0
x	0	x	0	x	0	0	1
x	0	0	1	x	0	0	x
x	0	0	x	x	0	1	0
x	0	0	x	0	1	x	0
x	0	0	x	0	x	0	1
0	1	0	x	0	x	0	x

Table 2: Values of S,R Flip-Flop inputs

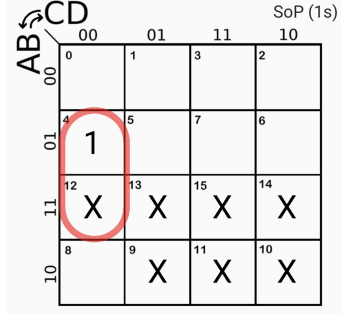
## 1.4 Simplified expressions for inputs using K-maps

Using K-maps, we get simplified expressions for  $S_i$  and  $R_i \forall i \in \{1, 2, 3, 4\}$  from the values obtained in Table 2, in terms of the inputs  $Q_i$  from Table 1.


**NOTE :** In the K-maps below,  $A = Q_3$ ,  $B = Q_2$ ,  $C = Q_1$  and  $D = Q_0$ .




(a) K-map for  $S_3$

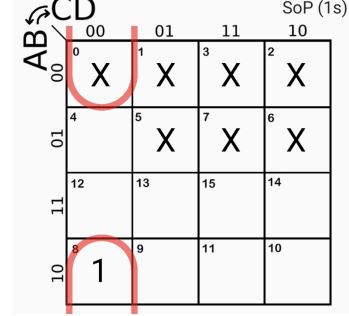

(b) K-map for  $R_3$

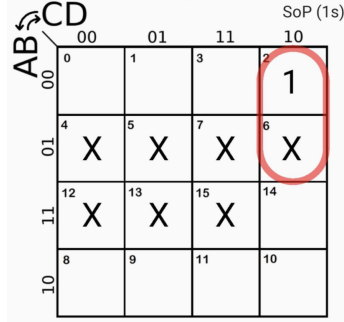


(c) K-map for  $S_2$

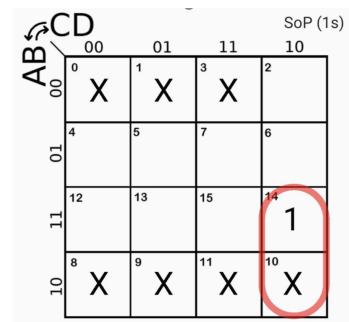

 
(d) K-map for  $R_2$

The simplified expressions obtained from the K-maps drawn above are as follows:


- $S_3 = Q_2 \bar{Q}_1 \bar{Q}_0$
- $R_3 = \bar{Q}_2 \bar{Q}_1 \bar{Q}_0$
- $S_2 = \bar{Q}_3 Q_1 \bar{Q}_0$
- $R_2 = Q_3 Q_1 \bar{Q}_0$




(a) K-map for  $S_1$

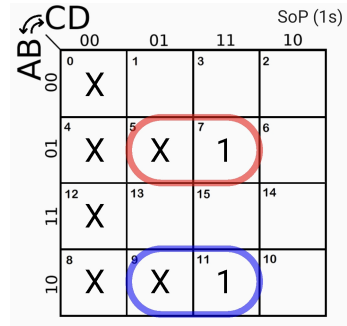

(b) K-map for  $R_1$

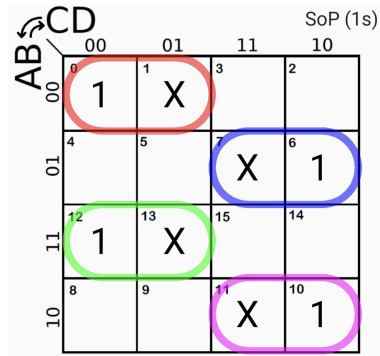

(c) K-map for  $S_0$

 

(d) K-map for  $R_0$

The simplified expressions obtained from the K-maps drawn above are as follows:

- $S_1 = Q_0 (\overline{Q_3} \oplus \overline{Q_2})$
- $R_1 = Q_0 (Q_3 \oplus Q_2)$
- $S_0 = \overline{Q_3 \oplus Q_2 \oplus Q_1}$
- $R_0 = Q_3 \oplus Q_2 \oplus Q_1$

## 1.5 Verilog Code

After getting the minimised expressions for all the inputs to SR-FFs, we write the following verilog code defining a module for gray code counter.

```
1 module srff ( q, qbar, qcur, s, r, clk, reset);
2     input s, r, clk, qcur, reset;
3     output reg q, qbar;
4     always @(reset == 1) begin // resets the output to 0
5         q = 0; qbar = 1;
6     end
```

```

7      always @(posedge clk) begin //positive edge triggered clock
8          if(s == 1 & r == 0) begin
9              q = 1; qbar = 0;
10         end
11         else if (s == 0 & r == 1) begin
12             q = 0; qbar = 1;
13         end
14         else if (s == 0 & r == 0) begin
15             q = qcur; qbar = ~qcur;
16         end
17     end
18 endmodule
19
20 module grayctr (
21     input [3 : 0] q,    //Takes in the 4-bit current state
22     input clk,
23     input reset,
24     output [3 : 0] qn  //Counter outputs the next state
25 );
26     wire qdash[0 : 3], s[0 : 3], r[0 : 3];
27     //Now we assign the inputs to SR-FFs in terms of the input
28     q.
29     assign s[3] = q[2] & (~q[1]) & (~q[0]);
30     assign r[3] = (~q[2]) & (~q[1]) & (~q[0]);
31     assign s[2] = (~q[3]) & q[1] & (~q[0]);
32     assign r[2] = q[3] & q[1] & (~q[0]);
33     assign s[1] = q[0] & (~(q[2] ^ q[3]));
34     assign r[1] = q[0] & (q[2] ^ q[3]);
35     assign s[0] = (~(q[3] ^ q[2] ^ q[1]));
36     assign r[0] = (q[3] ^ q[2] ^ q[1]);
37     //To implement the gray code counter, we call 4 SR-FF units
38     as follows :
39     srff FF1(qn[3], qdash[3], q[3], s[3], r[3], clk, reset);
40     srff FF2(qn[2], qdash[2], q[2], s[2], r[2], clk, reset);
41     srff FF3(qn[1], qdash[1], q[1], s[1], r[1], clk, reset);
42     srff FF4(qn[0], qdash[0], q[0], s[0], r[0], clk, reset);
43 endmodule

```

Here is the code for the test bench to simulate the 4-bit gray code counter:

```
1 module tb_grayctr;
2     reg [3 : 0] q;
3     reg clk;
4     reg reset;
5     wire [3 : 0] qn;
6     grayctr DUT( q, clk, reset, qn); // initialise the device
7     always #5 clk = ~clk;           // and the clock
8
9     initial begin
10         $dumpfile("grayctr.vcd");
11         $dumpvars(0, tb_grayctr);
12         $monitor($time, " Current state = %b  Next state = %b",
13             q, qn);
14         clk <= 0;
15         reset <=0;
16         q <= 4'b0000;
17         repeat(1) @(posedge clk) begin //reset the input and
18             the output
19             reset <=0;
20         end
21         repeat(31) @(posedge clk) begin //executes a full cycle
22             of the counter
23             q <= qn;
24         end
25         $finish;
26     end
27 endmodule
```

## 1.6 Output states and Waveform

Here is the output cycle of states generated using the test-bench:

```
Uddhavs-MacBook-Pro:ELL201 uddhavgoel$ iverilog -o grayctrsim grayctr.v tb_grayctr.v
Uddhavs-MacBook-Pro:ELL201 uddhavgoel$ vvp grayctrsim
VCD info: dumpfile grayctr.vcd opened for output.
    0 Current state = 0000 Next state = 0000
    5 Current state = 0000 Next state = 0001
   15 Current state = 0001 Next state = 0001
   25 Current state = 0001 Next state = 0011
   35 Current state = 0011 Next state = 0011
   45 Current state = 0011 Next state = 0010
   55 Current state = 0010 Next state = 0010
   65 Current state = 0010 Next state = 0110
   75 Current state = 0110 Next state = 0110
   85 Current state = 0110 Next state = 0111
   95 Current state = 0111 Next state = 0111
  105 Current state = 0111 Next state = 0101
  115 Current state = 0101 Next state = 0101
  125 Current state = 0101 Next state = 0100
  135 Current state = 0100 Next state = 0100
  145 Current state = 0100 Next state = 1100
  155 Current state = 1100 Next state = 1100
  165 Current state = 1100 Next state = 1101
  175 Current state = 1101 Next state = 1101
  185 Current state = 1101 Next state = 1111
  195 Current state = 1111 Next state = 1111
  205 Current state = 1111 Next state = 1110
  215 Current state = 1110 Next state = 1110
  225 Current state = 1110 Next state = 1010
  235 Current state = 1010 Next state = 1010
  245 Current state = 1010 Next state = 1011
  255 Current state = 1011 Next state = 1011
  265 Current state = 1011 Next state = 1001
  275 Current state = 1001 Next state = 1001
  285 Current state = 1001 Next state = 1000
  295 Current state = 1000 Next state = 1000
  305 Current state = 1000 Next state = 0000
  315 Current state = 0000 Next state = 0000
```

Figure 3: Outputs generated by the test bench

The figure below shows the waveform generated by the simulation of our 4-bit gray code counter :



Figure 4: Wave forms generated by the test bench

## 2 Synchronous Ring Counter

### 2.1 State Transition Table

Here is the state transition table for the synchronous ring counter given in the question:

Q3	Q2	Q1	Q0	D3	D2	D1	D0
0	0	0	1	1	0	0	0
1	0	0	0	0	1	0	0
0	1	0	0	0	0	1	0
0	0	1	0	1	0	0	1
1	0	0	1	1	1	0	0
1	1	0	0	0	1	1	0
0	1	1	0	1	0	1	1
1	0	1	1	0	1	0	1
0	1	0	1	1	0	1	0
1	0	1	0	1	1	0	1
1	1	0	1	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	1	1	1
0	1	1	1	0	0	1	1
0	0	1	1	0	0	0	1

Figure 5: State Table for Synchronous Ring Counter

### 2.2 Required Flip-Flops

From the state table we can clearly see that our ring counter traverses 15 states

⇒ Minimum number of Flip-Flops required =  $\lceil \log_2 15 \rceil = 4$

Since we need a D-flip flop to represent each bit and its transitions, we need **4 D-Flip flops** for our synchronous ring counter.

The values of the inputs to these D-Flip flops has been mentioned in the state table attached above.



## 2.3 Purpose of the counter

As we can clearly see from the state table, the counter doesn't cover all 16 states. **State 0000 is a forbidden state.**

The counter has 15 states, which all recur cyclically. Hence the purpose of the ring counter is to act like a **mod 15 counter**. As we can't see a set order in which the states appear, it can also be used as a **pseudo random sequence generator**, which can be used in security of data transmission.

Since we are going in a cycle, **the starting position doesn't matter**. All it does is shift the cycle a little bit.

## 2.4 Minimised expressions for inputs to D-Flip flops

Since the ring counter behaves like a shift register, the inputs to all the FFs, except the first one, is the output of the previous flip flop. Therefore, we get the minimised expressions for  $D_3$ ,  $D_2$ ,  $D_1$  and  $D_0$ . Here, I solve the K-map for  $D_3$  only, as it can not be directly deduced.

2.4.1  $D_2 = Q_3$

2.4.2  $D_1 = Q_2$

2.4.3  $D_0 = Q_1$

2.4.4  $D_3 = Q_0 \oplus Q_1$

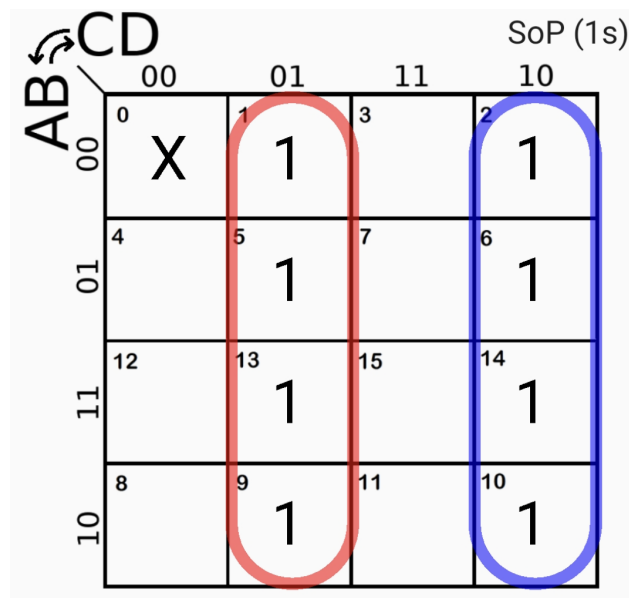


Figure 6: K-map for  $D_3$

**NOTE:** Here,  $A = Q_3$ ,  $B = Q_2$ ,  $C = Q_1$  and  $D = Q_0$ .

## 2.5 Verilog code

After getting the minimised expressions for all the inputs to D-FFs, we write the following verilog code defining a module for our synchronous ring counter.

```
1 module dff ( d, clk, qn, qnbar, reset);
2     input d, clk, reset;
3     output reg qn, qnbar;
4     always @(reset == 1) begin // resets the output to 0
5         qn = 0; qnbar = 1;
6     end
7     always @(posedge clk) begin // positive edge triggered
8         clock
9         if(d == 0) begin
10             qn = 0; qnbar = 1;
11         end
12         else begin
13             qn = 1; qnbar = 0;
14         end
15     end
16 endmodule
17 module ringctr (
18     input [3 : 0] q, // Takes in a 4-bit input
19     input clk,
20     input reset,
21     output [3 : 0] qn // Returns the next state (4-bit)
22 );
23     wire [3 : 0] qnbar;
24     //Here, we assign the inputs to D-FFs in terms of the
25     //input q, and call 4 units of D-FFs as follows :
26     dff #1 D1( q[0]^q[1], clk, qn[3], qnbar[3], reset);
27     dff #1 D2( q[3], clk, qn[2], qnbar[2], reset);
28     dff #1 D3( q[2], clk, qn[1], qnbar[1], reset);
29     dff #1 D4( q[1], clk, qn[0], qnbar[0], reset);
30 endmodule
```

Here is the code for the test bench to simulate our counter:

```
1 module tb_ringctr;
2     reg [3 : 0] q;
3     reg clk;
4     reg reset;
5     wire [3 : 0] qn;
6     ringctr DUT( q, clk, reset, qn);
7     //initialise the device under test
8     //and the clock
9     always #5 clk = ~clk;
10
11     initial begin
12         $dumpfile("ringctr.vcd");
13         $dumpvars(0, tb_ringctr);
14         $monitor($time, " Current state = %b Next state = %b",
15             q, qn);
16         //print the multiple states as outputs on positive
17         //clock edges
18         clk <= 0;
19         reset <= 0;
20         q <= 4'b0001;
21         //initialise the clk, reset, and input q
22         repeat(1) @(posedge clk) begin
23             reset <= 1;
24         end
25         //execute a full cycle of the counter as follows:
26         repeat(30) @(posedge clk) begin
27             q <= qn;
28         end
29         $finish;
30     end
31 endmodule
```

## 2.6 Output states and Waveform

Here is the output cycle of states generated using the test-bench:

```
Uddhavs-MacBook-Pro:ELL201 uddhavgoel$ iverilog -o ringctrsim ringctr.v tb_ringctr.v
Uddhavs-MacBook-Pro:ELL201 uddhavgoel$ vvp ringctrsim
VCD info: dumpfile ringctr.vcd opened for output.
    0 Current state = 0001 Next state = 0000
    5 Current state = 0001 Next state = 0000
   15 Current state = 1000 Next state = 1000
   25 Current state = 1000 Next state = 0100
   35 Current state = 0100 Next state = 0100
   45 Current state = 0100 Next state = 0010
   55 Current state = 0010 Next state = 0010
   65 Current state = 0010 Next state = 1001
   75 Current state = 1001 Next state = 1001
   85 Current state = 1001 Next state = 1100
   95 Current state = 1100 Next state = 1100
  105 Current state = 1100 Next state = 0110
  115 Current state = 0110 Next state = 0110
  125 Current state = 0110 Next state = 1011
  135 Current state = 1011 Next state = 1011
  145 Current state = 1011 Next state = 0101
  155 Current state = 0101 Next state = 0101
  165 Current state = 0101 Next state = 1010
  175 Current state = 1010 Next state = 1010
  185 Current state = 1010 Next state = 1101
  195 Current state = 1101 Next state = 1101
  205 Current state = 1101 Next state = 1110
  215 Current state = 1110 Next state = 1110
  225 Current state = 1110 Next state = 1111
  235 Current state = 1111 Next state = 1111
  245 Current state = 1111 Next state = 0111
  255 Current state = 0111 Next state = 0111
  265 Current state = 0111 Next state = 0011
  275 Current state = 0011 Next state = 0011
  285 Current state = 0011 Next state = 0001
  295 Current state = 0001 Next state = 0001
  305 Current state = 0001 Next state = 1000
```

Figure 7: Outputs generated by the test bench

The figure below shows the waveform generated by the simulation of our synchronous ring counter :

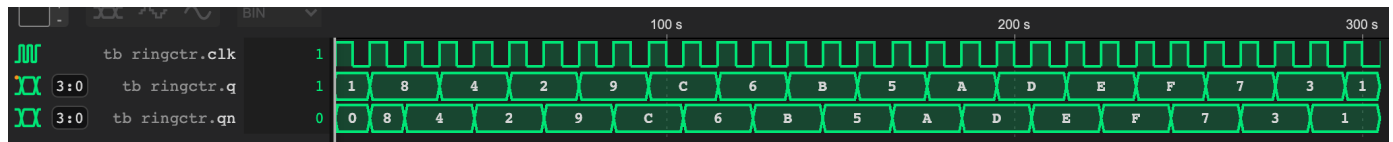



Figure 8: Wave forms generated by the test bench

### 3 Sequence Generator

Since my entry number is 2019EE10540, the output sequence that I need to generate is:

$$\{3\text{-bit binary of } (4\%8), 3\text{-bit binary of } (0\%8)\} = \{1,0,0,0,0,0\}$$

#### 3.1 State Transition Diagram

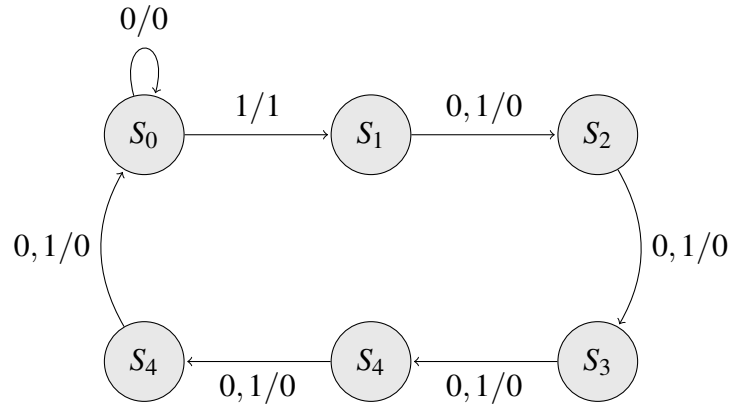

Here,  $S_0$  represents the idle state. The system starts in the idle state and on seeing the input 1, produces the output sequence Y, as mentioned above, irrespective of the input in the next 5 cycles.

#### 3.2 State Transition Table

Now, we encode our states of the FSM in binary form and obtain the following transition table:

$Q_2$	$Q_1$	$Q_0$	$X$	$Q_2^N$	$Q_1^N$	$Q_0^N$	$Y$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	0
0	0	1	1	0	1	0	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	0
0	1	1	0	1	0	0	0
0	1	1	1	1	0	0	0
1	0	0	0	1	0	1	0
1	0	0	1	1	0	1	0
1	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0

Table 3: State Transition Table for the Mealy machine given above

In the table given above,  $X$  represents the input,  $Y$  represents the output,  $Q_2Q_1Q_0$  represents the current state in 3-bit binary form, and finally  $Q_2^N Q_1^N Q_0^N$  represents the next state in 3-bit binary form.

**NOTE:** State  $S_0$  maps to 000,  $S_1$  maps to 001, and so on.

### 3.3 Flip-Flops required

The encoding of the states is done as follows:

- $S_0$  maps to 000
- $S_1$  maps to 001
- $S_2$  maps to 010
- $S_3$  maps to 011
- $S_4$  maps to 100
- $S_5$  maps to 101

Hence, we see that all the states can be encoded using 3 bits. Now, we also need 1 bit to represent the output,  $Y$ .

We need a total of **3 D Flip flops** to implement the given FSM, 1 for each bit to be encoded. The output  $Y$  can be implemented using simple combinational logic.


### 3.4 Minimised Expressions

Since we are using D-FFs, the bits used to represent the next state and the output are the same as the inputs to the D-FFs, i.e,


- $Q_2^N = D_2$
- $Q_1^N = D_1$
- $Q_0^N = D_0$

Using the K-maps shown below, we find the minimised expressions for  $D_2$ ,  $D_1$ ,  $D_0$  and  $Y$  in terms of the current state variables:  $Q_2$ ,  $Q_1$ ,  $Q_0$ , and the input  $X$ .

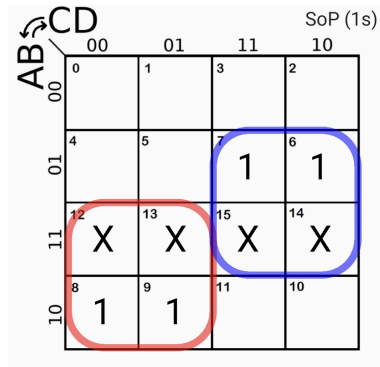
**NOTE :** In the K-maps below,  $A = Q_2$ ,  $B = Q_1$ ,  $C = Q_0$  and  $D = X$ .




(a) K-map for  $D_2$

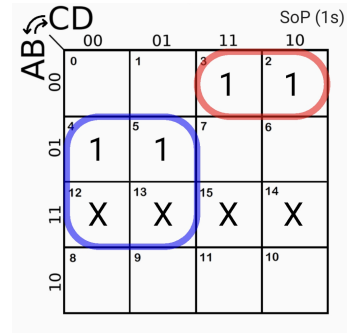

(b) K-map for  $D_1$

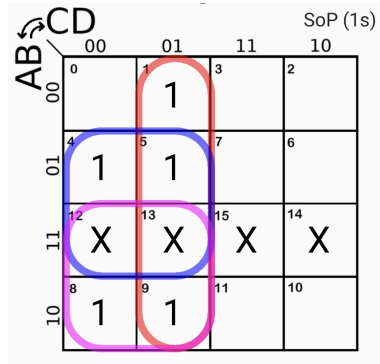

(c) K-map for  $D_0$

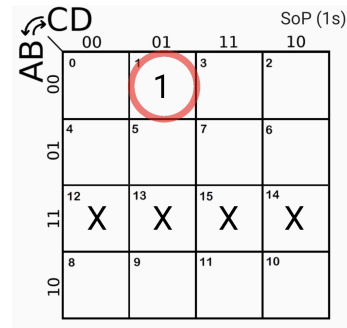

(d) K-map for  $Y$

The simplified expressions obtained from the K-maps drawn above are as follows:

- $D_2 = Q_2\bar{Q}_0 + Q_1Q_0$
- $D_1 = Q_1\bar{Q}_0 + \bar{Q}_2\bar{Q}_1Q_0$
- $D_0 = \bar{Q}_0 (Q_2 + Q_1 + X)$
- $Y = \bar{Q}_2\bar{Q}_1\bar{Q}_0X$

### 3.5 Verilog code

After getting the minimised expressions for all the inputs to D-FFs, we write the following verilog code defining a module for our synchronous ring counter.

```

1 module dff ( d, clk, qn, qnbar, reset);
2     input d, clk, reset;
3     output reg qn, qnbar;
4     always @(reset == 1) begin // resets the output to 0
5         qn = 0; qnbar = 1;
6     end

```

```

7      always @(posedge clk) begin // positive edge triggered
          clock
8          if(d == 0) begin
9              qn = 0; qnbar = 1;
10         end
11         else begin
12             qn = 1; qnbar = 0;
13         end
14     end
15 endmodule

16
17 module fsm (
18     input [2 : 0] q, // Takes in a 3-bit current state
19     input x_in, // Takes the input
20     input clk,
21     input reset,
22     output [2 : 0] qn, // Returns the next state (3-bit)
23     output y_out // Returns the output
24 );
25     wire qnbar [2 : 0], dd [2 : 0];
26     //Here, we assign the inputs to D-FFs in terms of the
27     //input x and the current state q :
28     assign dd[2] = (q[2] & (~q[0])) | (q[1] & q[0]);
29     assign dd[1] = (q[1] & (~q[0])) | ((~q[2]) & (~q[1]) & q
        [0]);
30     assign dd[0] = (~q[0]) & (q[2] | q[1] | x_in);
31     assign y_out = (~q[2]) & (~q[1]) & (~q[0]) & x_in;
32     //We call the 3 D-FF units as following to implement the
        FSM:
33     dff #1 D1( dd[2], clk, qn[2], qnbar[2], reset);
34     dff #1 D2( dd[1], clk, qn[1], qnbar[1], reset);
35     dff #1 D3( dd[0], clk, qn[0], qnbar[0], reset);
36 endmodule

```



Here is the code for the test bench to simulate our counter:

```
1 module tb_fsm;
2     reg [2 : 0] q;
3     reg x_in;
4     reg clk;
5     reg reset;
6     wire y_out;
7     wire [2 : 0] qn;
8     fsm DUT( q, x_in, clk, reset, qn, y_out);
9     //initialise the device under test
10    //and the clock
11    always #5 clk = ~clk;
12    always #40 x_in = ~x_in;
13
14    initial begin
15        $dumpfile("fsm.vcd");
16        $dumpvars(0, tb_fsm);
17        $monitor($time, " Current state = %b Next state = %b",
18            q, qn);
19        //print the multiple states as outputs on positive
20        //clock edges
21        clk <= 0;
22        x_in <= 1;
23        reset <= 0;
24        q <= 3'b000;
25        //initialise the clk, reset, and input q
26        repeat(30) @(posedge clk) begin
27            q <= qn;
28        end
29        $finish;
30    end
31 endmodule
```

### 3.6 Output states and Waveform

Here is the output cycle of states generated using the test-bench:

```
Uddhavs-MacBook-Pro:ELL201 uddhavgoel$ iverilog -o fsmsim fsm.v tb_fsm.v
Uddhavs-MacBook-Pro:ELL201 uddhavgoel$ vvp fsmsim
VCD info: dumpfile fsm.vcd opened for output.
      0 Current state = 000 Next state = 000
      5 Current state = 000 Next state = 001
     15 Current state = 001 Next state = 001
     25 Current state = 001 Next state = 010
     35 Current state = 010 Next state = 010
     45 Current state = 010 Next state = 011
     55 Current state = 011 Next state = 011
     65 Current state = 011 Next state = 100
     75 Current state = 100 Next state = 100
     85 Current state = 100 Next state = 101
     95 Current state = 101 Next state = 101
    105 Current state = 101 Next state = 000
    115 Current state = 000 Next state = 000
    165 Current state = 000 Next state = 001
    175 Current state = 001 Next state = 001
    185 Current state = 001 Next state = 010
    195 Current state = 010 Next state = 010
    205 Current state = 010 Next state = 011
    215 Current state = 011 Next state = 011
    225 Current state = 011 Next state = 100
    235 Current state = 100 Next state = 100
    245 Current state = 100 Next state = 101
    255 Current state = 101 Next state = 101
    265 Current state = 101 Next state = 000
    275 Current state = 000 Next state = 000
```

Figure 10: Outputs generated by the test bench

The figure below shows the waveform generated by the simulation of our Mealy Machine :

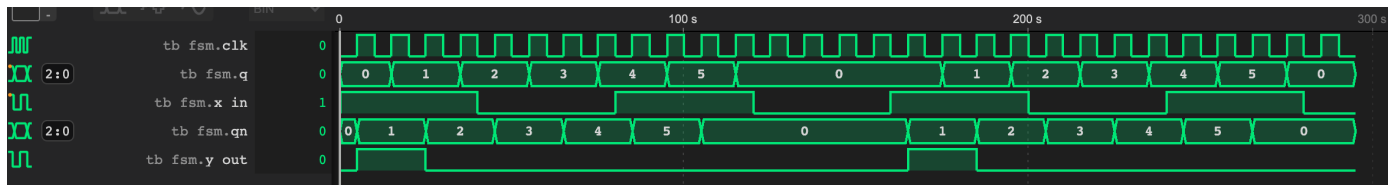


Figure 11: Wave forms generated by the test bench

Here we can see clearly, that when the FSM in the idle state, if the input is 0, then it stays in the idle state. If the input is 1, it starts generating the desired output sequence, irrespective of the input in the next 5 clock cycles.